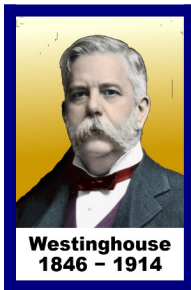


# Moving Electricity Efficiently



Westinghouse  
1846 - 1914

In 1896, **Westinghouse Electric** gave power to Buffalo, New York 26 miles (42 km) from Niagara Falls. Based on **Ohm's Law**, the design cut heat loss ( $P_{Loss} \downarrow$ ) by reducing the transmission current ( $I_{Tran} \downarrow$ ) across **power line** resistance ( $R_{Tran} \bullet$ ).

Based on **Ohm's Law**, the design cut heat loss ( $P_{Loss} \downarrow$ ) by reducing the transmission current ( $I_{Tran} \downarrow$ ) across **power line** resistance ( $R_{Tran} \bullet$ ).


$$\eta_{eff} \equiv (P_{Load} \bullet) / [(P_{Load} \bullet) + (P_{Loss} \downarrow)]$$

$$(P_{Loss} \downarrow) = (R_{Tran} \bullet)(I_{Tran} \downarrow)^2$$

$$(P_{Load} \bullet) = (V_{Tran} \uparrow)(I_{Tran} \downarrow) \eta_{eff}$$

For a set power ( $P_{Load} \bullet$ ), the reduced current ( $I_{Tran} \downarrow$ ) cut losses ( $P_{Loss} \downarrow$ ), driving efficiency ( $\eta_{eff}$ ) toward unity. The transmission voltage ( $V_{Tran} \uparrow$ ) was **stepped up** by **transformers** to meet the required load ( $P_{Load} \bullet$ ).

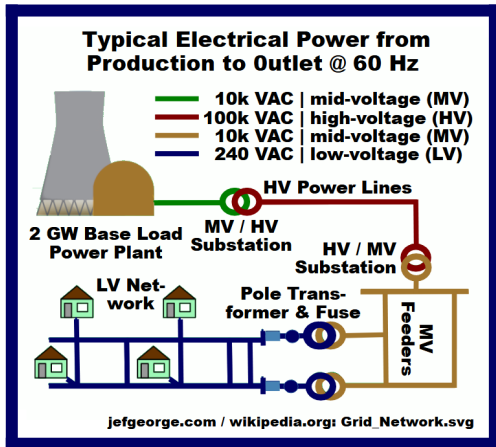[Wikipedia.org](https://en.wikipedia.org)



Copyright © 2024 [jefgeorge.com](http://jefgeorge.com)